

Analog & Digital VLSI Design

EEE/INSTR F313

Dept. of Electrical & Electronics Engineering (EEE)


Birla Institute of Technology & Science (BITS) Pilani

Hyderabad Campus

Problem 01


Perform the static timing analysis of the following circuit to

- (a) Determine the setup & hold violations, if the $f_\phi = 66.7$ MHz and the $t_H = t_S = 4$ ns at the capture FF.
- (b) What should be the maximum allowable t_H to prevent the hold violation?
- (c) What are the measures to resolve the setup violation?

 

Problem 02

- (a) Complete the PDN.
- (b) Identify the function F .
- (c) Size all the transistors so that the worst case delay is same as that of the symmetrical static CMOS inverter. Take $\mu_N = 2\mu_P$.

 


Problem 03

Implement the function $\overline{Y} = (A + B) \cdot C \cdot D$. Size the NFET and PFET devices such that the propagation delays are the same as the CMOS inverter with an NMOS with $(W/L)_N = 4$ and a PMOS with $(W/L)_P = 8$.

Problem 04

Calculate the switching activities of the following combinational functions, assuming equiprobable inputs:

 

Problem 05

Consider a processor which can operate in two different modes: (i) Mode 1: a high voltage mode (1 V, 3 GHz), and (ii) Mode 2: a low voltage mode (0.75 V, 2 GHz). What is the ratio of switching power consumption of mode 1 : mode 2?