
 


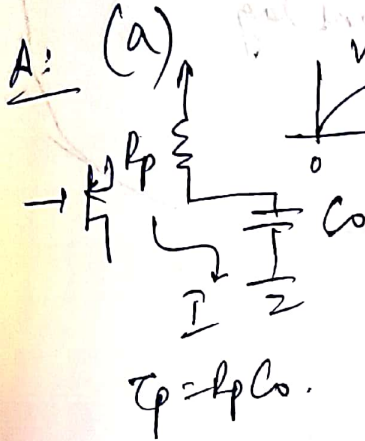- ① Derive exp. for (a) rise time, (b) fall time, (c) propagation delay using transient analysis of basic RC networks, where the nFETs & pFETs are approx. as linear resistors with resistances  $R_n = \frac{1}{\beta_n V_{ov}}$  &  $R_p = \frac{1}{\beta_p V_{ov}}$ . ~~At this~~  
Derive exp. using both diff. eqns and LT formulations.



$$\frac{V_{dd} - V_0}{R_p} = + C_o \frac{dV_0}{dt}$$

$$1 - \frac{V_0}{V_{dd}} = e^{-t/\tau_p}$$

$$\boxed{\begin{aligned} V_0(t) &= V_{dd}(1 - e^{-t/\tau_p}) \\ p'(x) + q(x)e^{\lambda x} &= f(x) \end{aligned}}$$

$$\frac{V_{dd}}{s} - V_0(s) = + R_p C_o \left[ s V_0(s) - \underbrace{V_0(t=0)}_{V_0} \right]$$

$$\frac{V_{dd}}{s} = V_0(s) [1 + s R_p C_o]$$

$$\int_0^{V_{dd}} \frac{dV_0}{V_0 - V_{dd}} = -\frac{1}{R_p C_o} \int_0^t dt \ln \left( \frac{V_0 - V_{dd}}{-V_{dd}} \right) = \frac{+t}{R_p C_o}$$

$$\frac{V_{dd}}{s} = V_0(s) [1 + s R_p C_o]$$

$$V_0(s) = V_{dd} \left( \frac{1}{s} - \frac{1}{s + \frac{1}{R_p C_o}} \right)$$

Operational calc.


$$V_0(s) = \frac{V_{dd}}{s(s + \frac{1}{R_p C_o})} \quad \therefore \frac{1}{R_p C_o}$$

$$V_0(t) = V_{dd} (1 - e^{-t/\tau_p})$$

$$F(j\omega) = \int_0^{\infty} f(t) e^{-j\omega t} dt$$

$$L(s) = \int_0^{\infty} f(t) e^{-st} dt$$


$s = \sigma + j\omega$

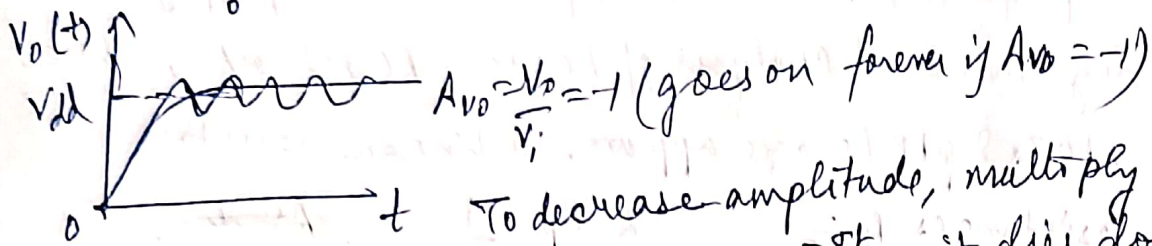

To decrease amplitude, multiply it with  $e^{-\sigma t}$ . it dies down.

We use  $\sigma$  & not  $j\omega$  cause  $+j\omega$  means lead &  $-j\omega$  means lag  
(damping factor)

 
$$L(s) = \int_0^{\infty} f(t) e^{-(\sigma + j\omega)t} dt$$



$$f_{max} = \frac{1}{t_r + t_f}$$

If  $\sigma$  is very high,  $t_r$  &  $t_f$  are very high &  $f_{max}$  becomes very low.

 (b)  $V_o(t) = V_{dd} e^{-t/R_n C_o}$  (pull down  $n(\omega)$ )



$$V_o(t) \equiv V_{dd} \rightarrow 0$$

$$\frac{V_o}{R_n} = -C_n \frac{dV_o}{dt}$$

$$\Rightarrow V_o(s) = -R_n C_o \left[ s V_o(s) - \underbrace{V_o(t=0)}_{V_{dd}} \right]$$

$$= -R_n C_o [s V_o(s) - V_{dd}]$$

$$\Rightarrow V_o(s) [1 + s R_n C_o] = R_n C_o V_{dd}$$

$$\Rightarrow V_0(s) = \frac{V_{dd}}{s + \frac{1}{R_n C_0}} \Rightarrow \left[ V_0(t) = V_{dd} e^{-t/R_n C_0} \right]$$

For ~~0.9 V<sub>dd</sub>~~ for fall time,

$$0.9 V_{dd} = V_{dd} e^{-t_1/R_n C_0}$$

$$0.1 V_{dd} = V_{dd} e^{-t_2/R_n C_0}$$

$$9 = e^{(t_2 - t_1)/R_n C_0}$$

$$t_p = t_2 - t_1 = \tau_n \ln 9$$

For propagation delay take 0.5 & 0.1,

$$0.5 V_{dd} = V_{dd} e^{-t_1/R_n C_0}$$

$$0.1 V_{dd} = V_{dd} e^{-t_2/R_n C_0}$$

$$5 = e^{(t_2 - t_1)/R_n C_0}$$


$$t_p = t_2 - t_1 = \tau_n \ln 5$$

Q2:

The transistors in the static CMOS inverter can be modeled as constant linear resistors (when turned on)  $V_{DD} = 2.5V$ ,  $C_L = 25pF$ . As usual, assume input signal has a very steep slope and is stable before the out starts to switch.

(a) For a 1 → 0 transition at the i/p, determine the transistor resistances that will result in a 10% → 90% of  $V_{DD}$  transition of the o/p within 5ns.

 (b) Draw rough sketch of current drawn from the power supply as a function of time during this low-to-high transition & derive the appropriate eqns. that describe the behavior.






A:  $V_{DD} = 2.5V$ ,  $C_L = 25 pF$ .

(a)  $t_{\tau} = t_p (\ln 9)$   $s_n = R_p \times 25 pF \times 2.2$   
 $\Rightarrow R_p = \frac{90.91 \Omega}{2.2}$


(b)  $V_o(t) = V_{dd} (1 - e^{-t/\tau_p})$


$I_o(t) = \frac{V_{dd} - V_o}{R_p} = \frac{V_{dd}}{R_p} e^{-t/\tau_p} = \frac{2.5}{90.91} e^{-t/(5n/2.2)}$

$= 27.49 e^{-t/(2.27n)} mA$

 

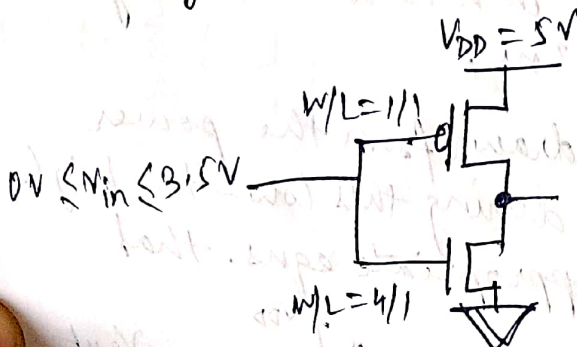Q3 In the adjoining static CMOS inverter, assume  $V_{DD} \approx V_{DD} = 5V$ ,  $\mu_n C_{ox} = 500 \mu A/V^2$ ,  $\mu_p C_{ox} = 200 \mu A/V^2$ ,  $V_{TN} = -V_{TP} = 1V$ .  $I_P$  is varied within the range  $0 \leq V_{in} \leq 3.5V$ . Compute the value of  $V_{OL}$ .



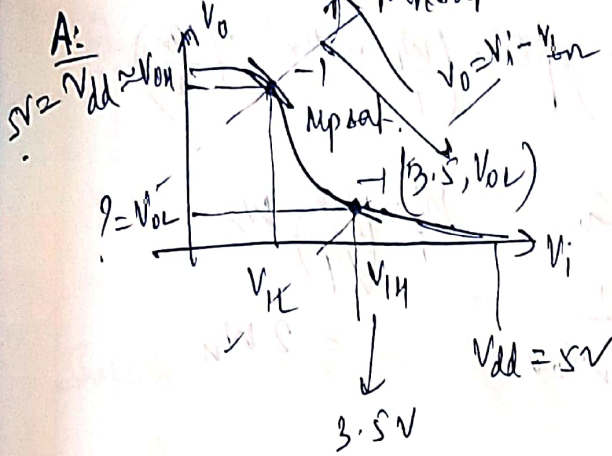

@  $(V_{IH}, V_{OL})$ ,  $M_n$  lin.,  $M_p$  sat.

$$\beta_n \left( V_{OVn} - \frac{V_{dsn}}{2} \right) V_{dsn} = \frac{\beta_p}{2} V_{ovp}^2$$

$$\beta_n \left( V_{IH} - V_{tn} - \frac{V_{OL}}{2} \right) V_{OL}$$

$$= \frac{\beta_p}{2} (V_{DD} - V_{IH} - V_{tp})^2$$

Sub values -

$$200 \mu A \times 4 \times \left( 3.5 - 1 - \frac{V_{OL}}{2} \right) V_{OL} = 200 \mu A \times 1 \times (5 - 3.5 - 1)^2$$


$$\Rightarrow 0 = \frac{V_{OL}^2}{2} - 2.5 V_{OL} + 0.0125$$

$$\Rightarrow V_{OL} = \begin{cases} 4.99V \\ 5mV \end{cases} \rightarrow \text{supposed to be very close to 0.}$$

~~Q4~~

Q4 Design (a) NOR<sub>2</sub> gate and (b) NAND<sub>3</sub> gate with rise & fall times same as the symmetrical static CMOS inverter at the same tech made with min delay

Take  $\mu_n = 2\mu_p$ .

 

$$\beta_p = \beta_n \rightarrow \mu_p C_{ox} \left( \frac{W_p}{L} \right) = \mu_n C_{ox} \left( \frac{W_n}{L} \right)$$

$$\tau_p = \tau_n$$

$$R_p C_o = R_n C_o$$

$$\frac{1}{\beta_p V_{ov}} = \frac{1}{\beta_n V_{ov}}$$

$$W_p = \left( \frac{\mu_n}{\mu_p} \right) W_n = 2W_n$$


$$t_{gr} = 2.2 \tau_{pH}$$

$$t_{gr} = 2.2 \tau_n$$

(b)

NAND

$y = A \cdot B = \text{series}$

 

$$\frac{2}{\beta_n' V_{ov}} = \frac{1}{\beta_n V_{ov}}$$

$$\Rightarrow \beta_n' = 2\beta_n$$

$$\Rightarrow \frac{2}{\mu_n \frac{W_n'}{L}} = \frac{1}{\mu_n \frac{W_n}{L}}$$

$$\Rightarrow W_n' = 2W_n$$

$$\beta_p' = \beta_p$$

$$\beta_p' = \beta_p$$

$$\mu_p (W_p') = \mu_p (W_p)$$