

Analog & Digital VLSI Design

EEE/INSTR F313

Fall Semester 2025


Surya Shankar Dan & Syed Ershad Ahmed

Tutorial 13

Department of Electrical and Electronics Engineering (EEE)
Birla Institute of Technology and Science (BITS) Pilani
Hyderabad Campus


Problem 1

Calculate the small signal voltage gain A_v and output resistance R_{out} of circuit. Given: $V_{DD} = 12\text{ V}$, $R_1 = 162\text{ k}\Omega$, $R_2 = 463\text{ k}\Omega$, $R_S = 0.75\text{ k}\Omega$, $R_{sig} = 4\text{ k}\Omega$, $V_t = 1.5\text{ V}$, $\beta = 1\text{ mA/V}^2$, $\lambda = 0.01\text{ /V}$.

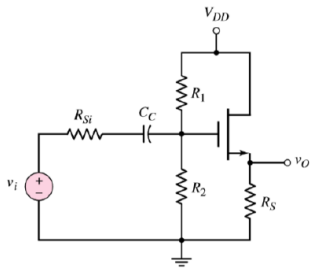


Problem 2

Given: $V_{DD} = 20\text{ V}$, $V_t = -2\text{ V}$, $\mu_p C_{ox} = 40\text{ }\mu\text{A/V}^2$, $\lambda = 0$, $R_{sig} = 4\text{ k}\Omega$. Design a circuit such that $V_{SDQ} = 10\text{ V}$, $I_{SQ} = 2.5\text{ mA}$, $R_{in} = 50\text{ k}\Omega$, and the transistor (W/L) ratio is such that the small signal voltage gain is $A_v = 0.9\text{ V/V}$.

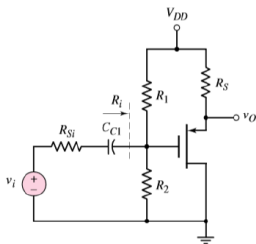

Problem 3

Determine the output voltage gain for a given input current. Given: $I_Q = 1$ mA, $V_+ = 5$ V, $V_- = -5$ V, $R_G = 100$ k Ω , $R_D = 4$ k Ω , $R_{si} = 50$ k Ω and $R_L = 10$ k Ω , $V_t = 1$ V, $\beta = 2$ mA/V², $\lambda = 0$, and the input current is $100 \sin(\omega t)$ μ A.

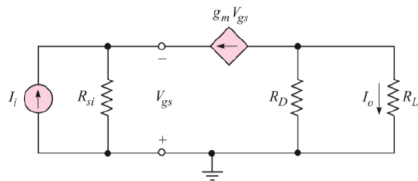

Problem 4

For the following differential amplifier, determine the DC voltages at nodes A and B. Also calculate the small signal differential gain for the amplifier. Assume no channel length modulation, no body effect, all transistors are operating in saturation region, $\mu_n C_{ox} = 200 \mu\text{A}/\text{V}^2$, $V_t = 1 \text{ V}$.

