

# **Analog & Digital VLSI Design**

**EEE/INSTR F313**

Dept. of Electrical & Electronics Engineering (EEE)

Birla Institute of Technology & Science (BITS) Pilani

Hyderabad Campus

## Problem 01

A static CMOS inverter with minimum sized FETs has  $\beta_N = 0.2 \text{ mA/V}^2$ ,  $\beta_P = 0.1 \text{ mA/V}^2$ ,  $V_{TN} = -V_{TP} = 0.6 \text{ V}$ , and  $V_{DD} = 3.3 \text{ V}$ .

- (a) What is the inverter switching threshold  $V_M$ ?
- (b) What is the resistance for each FETs?
- (c) What are the rise and fall times of the circuit if the output node parasitic capacitance is 9 fF, ignoring any load?
- (d) As a consequence, estimate the maximum operating frequency of the circuit.
- (e) What are the propagation delays for an additional load of 25 fF?


## Problem 02

A certain circuit has a datapath (5, 4) and a clockpath (4.5, 4.1). Find the setup and hold times of the circuit, given that the (max, min) denote the maximum and minimum propagation delays in ns.

## Problem 03

Perform the static timing analysis of the following circuit to

 - (a) Determine the setup & hold violations, if the  $f_\phi = 66.7$  MHz and the  $t_H = t_S = 4$  ns at the capture FF.
- (b) What should be the maximum allowable  $t_H$  to prevent the hold violation?
- (c) What are the measures to resolve the setup violation?



## Problem 04

- (a) Complete the PDN.
- (b) Identify the function  $F$ .
- (c) Size all the transistors so that the worst case delay is same as that of the symmetrical static CMOS inverter. Take  $\mu_N = 2\mu_P$ .

