

Analog & Digital VLSI Design

EEE/INSTR F313

Fall Semester 2025

Surya Shankar Dan

Tutorial 01

Department of Electrical and Electronics Engineering (EEE)
Birla Institute of Technology and Science (BITS) Pilani
Hyderabad Campus

Problem 1

List the VLSI industry technology nodes below 1 μm , following the ITRS roadmap.

Problem 2

Find the on resistance of an nMOS transistor if $V_{ds} = 1.8$ V, $V_{gs} = 1.2$ V, and $V_{bs} = -1$ V. Assume $W/L = 10$, $V_{t0} = 0.45$ V, body effect coefficient $\gamma = 0.4$, $\mu_n C_{ox} = 300$ $\mu\text{A}/\text{V}^2$, and the Fermi potential of the Si substrate is $|\phi_F| = 0.3$ V.

Problem 3


For an nMOS transistor with $R_{on} = 600\ \Omega$ and the load resistance $R_L = 6\ \text{k}\Omega$, find out the output voltage when the input is high ($V_{dd} = 5\ \text{V}$). Comment on the values of R_L .

Problem 4

Under what conditions will the following pMOS and nMOS transistors turn on?




(a)

 

(b)

Problem 5

- (a) Estimate the frequency of the output signal V_{out} of the oscillator circuit shown below, given that the propagation delay $t_p = 30$ ns.
- (b) What will be the frequency if we add another inverter to the chain?

 

Problem 6

Determine the modes of operation (saturation, linear, or cutoff) and the corresponding drain current I_D for each of the following biasing configurations: (a) Given: nMOS $k'_n = 115 \mu\text{A}/\text{V}^2$, $V_{tn0} = 0.43 \text{ V}$, $\lambda_n = 0.06 / \text{V}$, pMOS $k'_p = 30 \mu\text{A}/\text{V}^2$, $V_{tp0} = -0.4 \text{ V}$, $\lambda_p = -0.1 / \text{V}$. Assume $W/L = 1$ for all devices.

(a) nMOS $V_{gsn} = 2.5 \text{ V}$, $V_{dsn} = 2.5 \text{ V}$, pMOS $V_{gsp} = -0.5 \text{ V}$, $V_{dsp} = -1.25 \text{ V}$

(b) nMOS $V_{gsn} = 3.3 \text{ V}$, $V_{dsn} = 2.2 \text{ V}$, pMOS $V_{gsp} = -2.5 \text{ V}$, $V_{dsp} = -1.8 \text{ V}$

(c) nMOS $V_{gsn} = 0.6 \text{ V}$, $V_{dsn} = 0.1 \text{ V}$, pMOS $V_{gsp} = -2.5 \text{ V}$, $V_{dsp} = -0.7 \text{ V}$